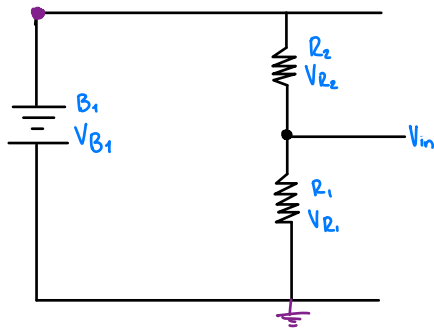


Voltimeter




$$V_{B1} = V_{in} \left(1 + \frac{R_2}{R_1} \right)$$


$$R_2 = \frac{V_{B1} - V_{in}}{V_{in}/R_1}$$

$$V_{in} = 3.1$$

Frecuencia

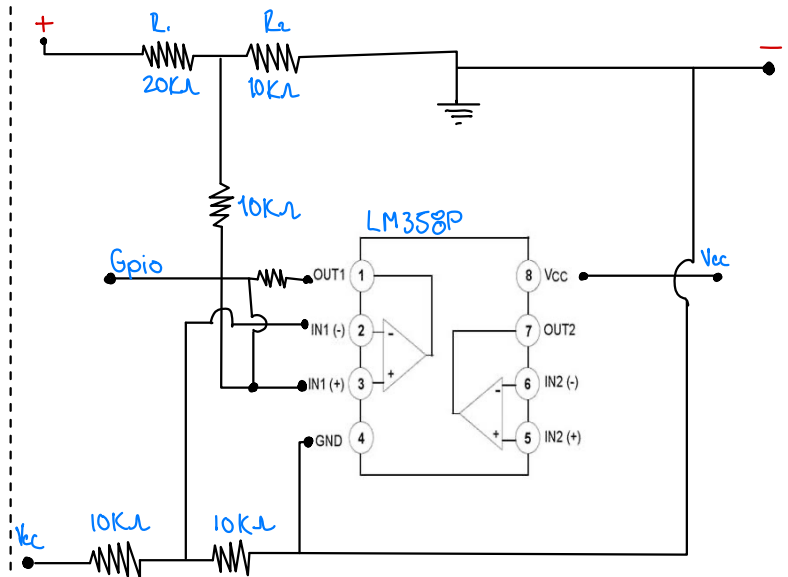


Capacitance meter

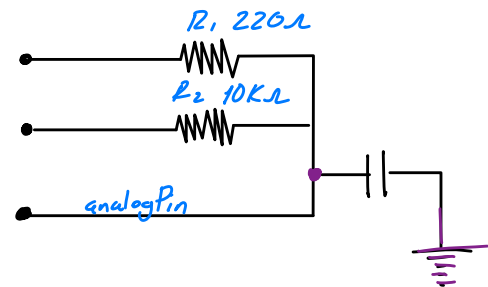

$$C = \frac{\text{Time} \rightarrow 63.2\% \text{ de } ADC = 2588}{R}$$


Resistance meter
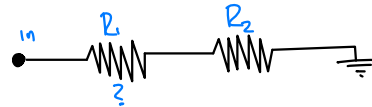
$$V_{out} = \frac{V_{in} \cdot R_2}{R_1 + R_2} \approx R_1 = R_2 \left(\frac{V_{in}}{V_{out}} - 1 \right)$$



Range	0-100	100-1k	1k-10k	10k-100k
R2	100 ohms	1k ohms	10k ohms	100k ohms

Amperimeter

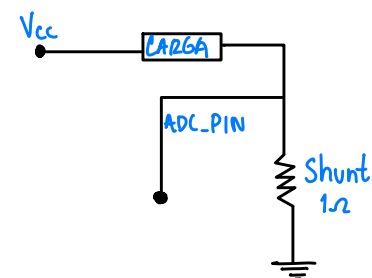

$$I = \frac{V}{R}$$

Continuidad

